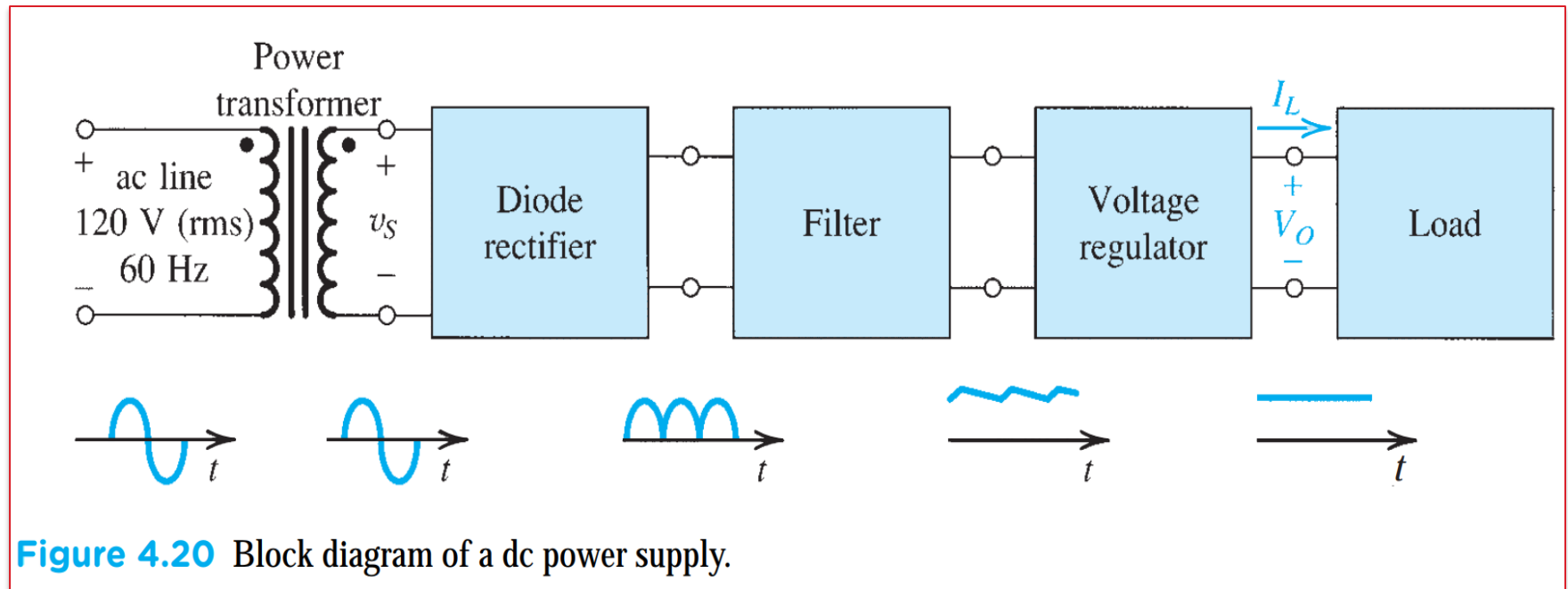


# Diode Applications

## Rectifier Circuits


One of the most important applications of diodes is in the design of rectifier (AC to DC) circuits. A diode rectifier forms an essential building block of the dc power supplies required to power electronic equipment. A block diagram of such a power supply is shown in Fig. 4.20.



# Diode Applications

## The Half-Wave Rectifier

The half-wave rectifier utilizes alternate half-cycles of the input sinusoid. Figure 4.21(a) shows the circuit of a half-wave rectifier. Figure 4.21(b) shows the output voltage obtained when the input  $v_s$  is a sinusoid.

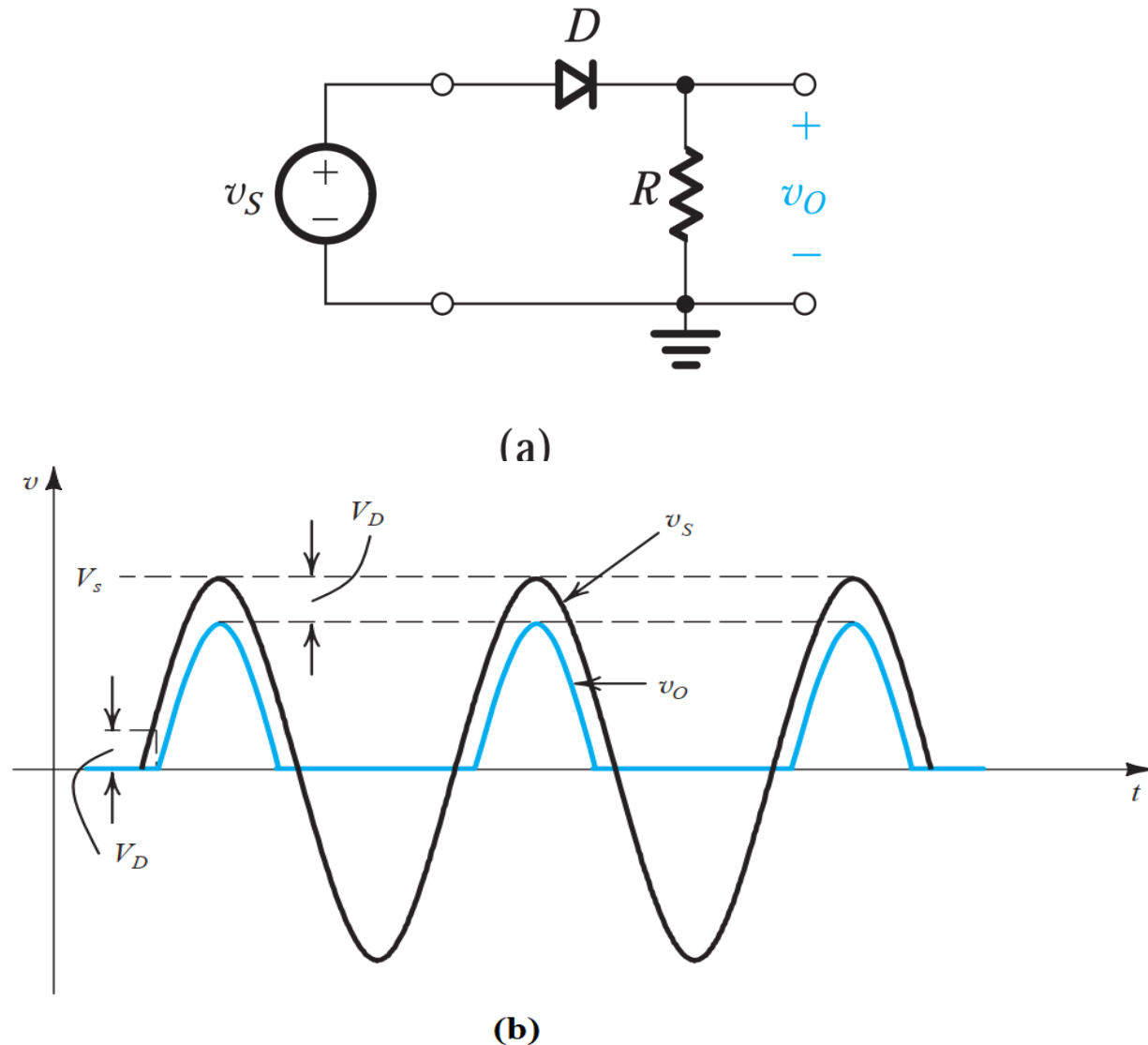


**Figure 4.21** (a) Half-wave rectifier. (b) Input and output waveforms.

# Diode Applications

## The Full-Wave Rectifier

The full-wave rectifier utilizes both halves of the input sinusoid. To provide a unipolar output, it inverts the negative halves of the sine wave. One possible implementation is shown in Fig. 4.22(a). Here the transformer secondary winding is **center-tapped** to provide two equal voltages  $v_S$  across the two halves of the secondary winding with the polarities indicated.

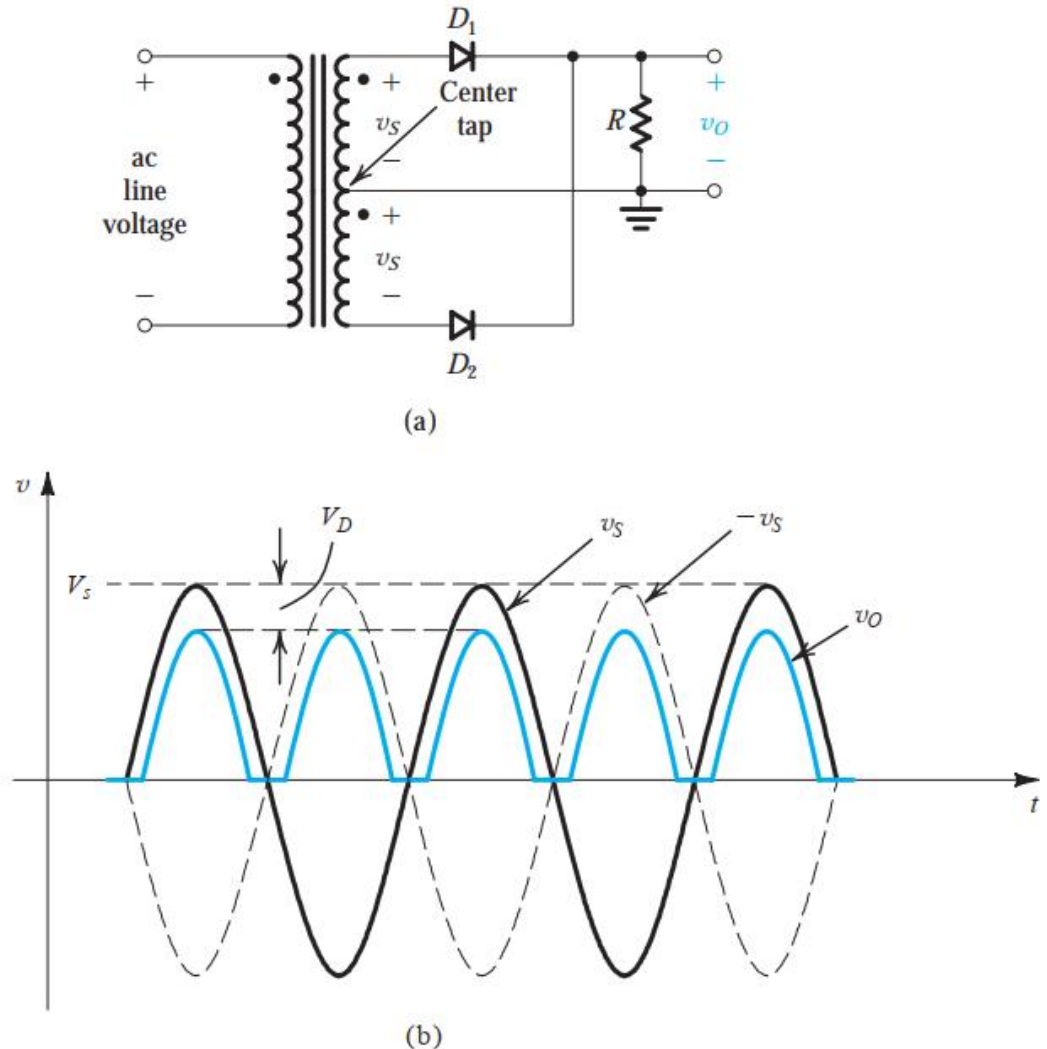

**Figure 4.22** Full-wave rectifier utilizing a transformer with a center-tapped secondary winding: (a) circuit; (b) input and output waveforms.

# Diode Applications

**The Center-Tapped rectifier circuit operates as follows:**


Note that when the input line voltage (feeding the primary) is positive, both of the signals labeled  $v_s$  will be positive. In this case  $D_1$  will conduct and  $D_2$  will be reverse biased. The current through  $D_1$  will flow through R and back to the center tap of the secondary. The circuit then behaves like a half-wave rectifier.

Now, during the negative half-cycle of the ac line voltage, both of the voltages labeled  $v_s$  will be negative. Thus  $D_1$  will be cut off while  $D_2$  will conduct. The current conducted by  $D_2$  will flow through R and back to the center tap. It follows that during the negative half-cycles while  $D_2$  conducts, the circuit behaves again as a half-wave rectifier. The important point, however, is that the current through R always flows in the same direction, and thus  $v_o$  will be unipolar, as indicated in Fig. 4.22(b).

# Diode Applications

## The Bridge Rectifier

An alternative application of the full-wave rectifier is shown in Fig. 4.23(a). This circuit, known as the **bridge rectifier** because of the similarity with the Wheatstone bridge, does not require a center-tapped transformer, a distinct advantage over the center-tapped rectifier circuit of Fig. 4.22. The bridge rectifier, requires four diodes as compared to two in the previous circuit. This is not much of a disadvantage, because diodes are inexpensive.

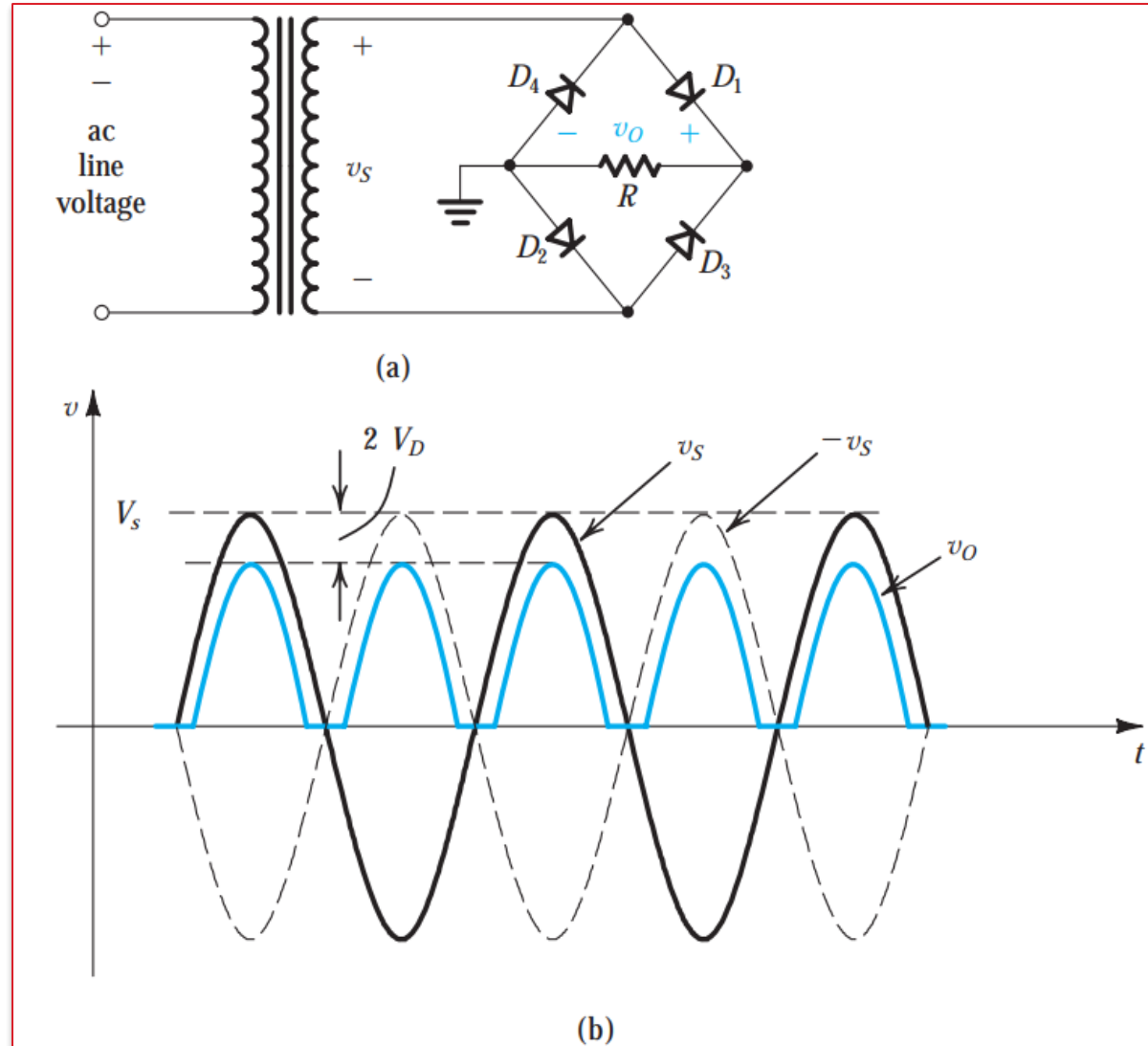

**Figure 4.23** The bridge rectifier: (a) circuit; (b) input and output waveforms.

# Diode Applications

**The bridge rectifier circuit operates as follows:**

During the positive half-cycles of the input voltage,  $v_s$  is positive, and thus current is conducted through diode  $D_1$ , resistor  $R$ , and diode  $D_2$ . Meanwhile, diodes  $D_3$  and  $D_4$  will be reverse biased. Observe that there are two diodes in series in the conduction path, and thus  $v_o$  will be lower than  $v_s$  by two diode drops (compared to center-tapped). This is somewhat of a disadvantage of the bridge rectifier.



Next, consider the situation during the negative half-cycles of the input voltage. The secondary voltage  $v_s$  will be negative, and thus  $-v_s$  will be positive, forcing current through  $D_3$ ,  $R$ , and  $D_4$ . Meanwhile, diodes  $D_1$  and  $D_2$  will be reverse biased. The important point to note, though, is that during both half-cycles, current flows through  $R$  in the same direction (from right to left), and thus  $v_o$  will always be positive, as indicated in Fig. 4.23(b).

# Diode Rectifier

The average value of Half wave rectifier circuit

$$\begin{aligned} V_o &= \frac{1}{T} \int_0^T v(t) dt \\ &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta \\ &= \frac{V_m}{2\pi} \left[ \int_0^{\pi} \sin \theta d\theta + \int_{\pi}^{2\pi} \sin \theta d\theta \right] \\ &= \frac{V_m}{2\pi} [-\cos \theta]_0^{\pi} \\ &= -\frac{V_m}{2\pi} [-1 - 1] = \frac{V_m}{2\pi} [2] \\ \therefore V_o &= \frac{V_m}{\pi} \end{aligned}$$
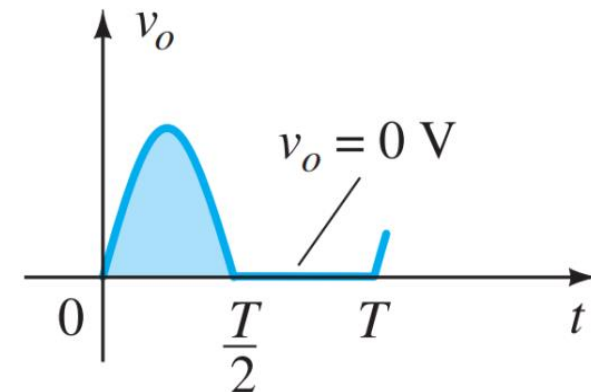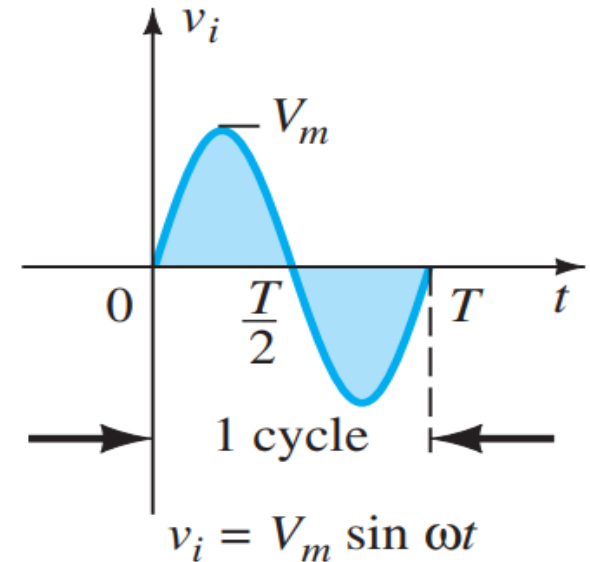
$$\text{Similarly, } I_o = \frac{I_m}{\pi}$$



# Diode Rectifier

The R.M.S value of Half wave rectifier circuit,

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{T} \int_0^T \{v(t)\}^2 dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \theta d\theta} \\ &= \sqrt{\frac{V_m^2}{2\pi} [\int_0^\pi \sin^2 \theta d\theta + \int_\pi^{2\pi} \sin^2 \theta d\theta]} \\ &= \sqrt{\frac{V_m^2}{2\pi} \int_0^\pi \sin^2 \theta d\theta} = \sqrt{\frac{V_m^2}{4\pi} \int_0^\pi 2\sin^2 \theta d\theta} \\ &= \sqrt{\frac{V_m^2}{4\pi} \int_0^\pi (1 - \cos 2\theta) d\theta} = \sqrt{\frac{V_m^2}{4\pi} \left\{ \int_0^\pi (1) d\theta - \int_0^\pi (\cos 2\theta) d\theta \right\}} \\ &= \sqrt{\left( \frac{V_m^2}{4\pi} \times [\theta]_0^\pi \right)} = \sqrt{\left( \frac{V_m^2}{4\pi} \times \pi \right)} = \sqrt{\left( \frac{V_m^2}{4} \right)} \end{aligned}$$

$$V_{rms} = \frac{V_m}{2}$$

$$\text{Similarly, } I_{rms} = \frac{I_m}{2}$$




# Diode Rectifier

The average value of Full wave rectifier circuit

$$\begin{aligned} V_o &= \frac{1}{2\pi} \int_0^{2\pi} v(t) dt \\ &= \frac{1}{2\pi} \left[ \int_0^{\pi} V_m \sin\theta d\theta + \int_{\pi}^{2\pi} V_m \sin\theta d\theta \right] \\ &= \frac{1}{\pi} \int_0^{\pi} V_m \sin\theta d\theta = \frac{V_m}{\pi} [-\cos\theta]_0^{\pi} \\ &= -\frac{V_m}{\pi} [-1 - 1] \end{aligned}$$

$$V_o = \frac{2V_m}{\pi}$$
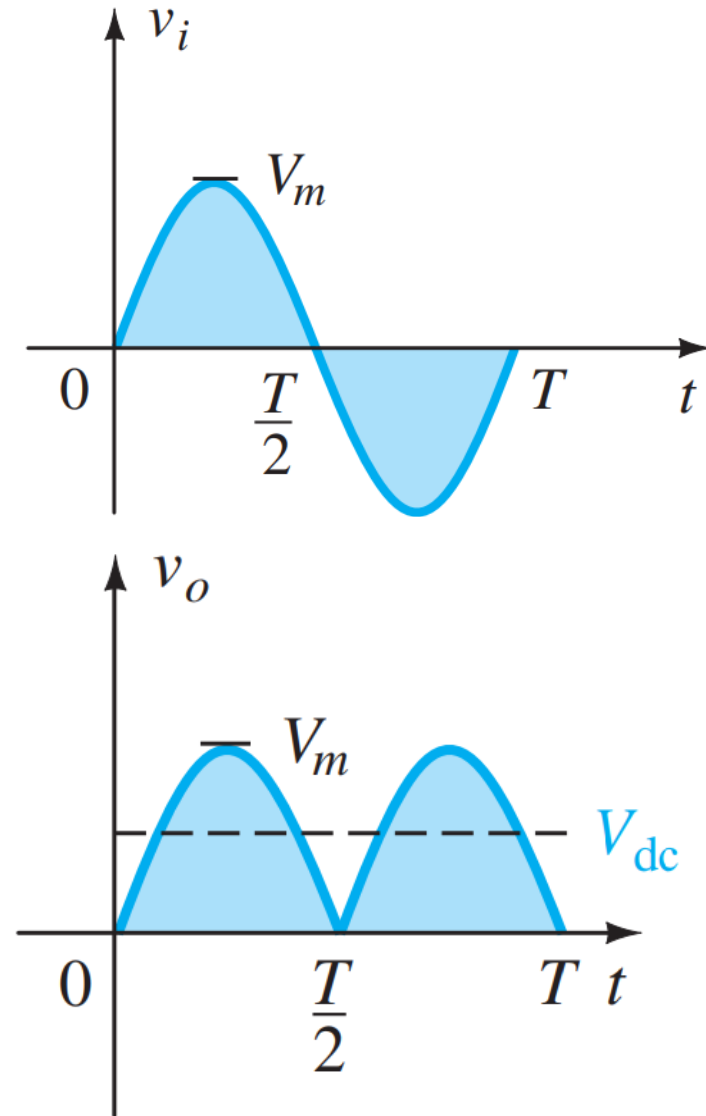
$$\text{Similarly, } I_o = \frac{2I_m}{\pi}$$



# Diode Rectifier

The RMS value of full wave rectifier circuit,

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} \{v(t)\}^2 d\theta}$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} 2\sin^2 \theta d\theta}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[ \left( \theta - \frac{\sin 2\theta}{2} \right) \right]_0^{\pi}} = \sqrt{\frac{V_m^2}{2\pi} \times \pi}$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\text{Similarly, } I_{rms} = \frac{I_m}{\sqrt{2}}$$

# Diode Rectifier

Efficiency of Half wave rectifier

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{dc}}{P_{ac}} = \frac{P_{avg}}{P_{rms}}$$

$$P_{dc} = I_o^2 \times R = \left(\frac{I_m}{\pi}\right)^2 \times R_L$$

$$\text{Since } I_o = \frac{I_m}{\pi}$$

$$P_{ac} = I_{rms}^2 \times R = \left(\frac{I_m}{2}\right)^2 \times (R_L + r_f) \cong \left(\frac{I_m}{2}\right)^2 \times R_L$$

$$\text{Since } I_{rms} = \frac{I_m}{2}$$

$$\therefore \eta = \frac{P_{dc}}{P_{ac}} = \frac{\left(\frac{I_m}{\pi}\right)^2 \times R_L}{\left(\frac{I_m}{2}\right)^2 \times R_L} = \frac{4}{\pi^2} = 0.405 = \mathbf{40.5\%}$$

# Diode Rectifier

Efficiency of Full wave rectifier

$$\eta = \frac{P_{out}}{P_{in}} = \frac{P_{dc}}{P_{ac}} = \frac{P_{avg}}{P_{rms}}$$

$$P_{dc} = I_o^2 \times R = \left(\frac{2I_m}{\pi}\right)^2 \times R_L$$

$$\text{Since } I_o = \frac{2I_m}{\pi}$$

$$P_{ac} = I_{rms}^2 \times R = \left(\frac{I_m}{\sqrt{2}}\right)^2 \times (R_L + 2r_f) \cong \left(\frac{I_m}{2}\right)^2 \times R_L$$

$$\text{Since } I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\therefore \eta = \frac{P_{dc}}{P_{ac}} = \frac{\left(\frac{2I_m}{\pi}\right)^2 \times R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times R_L} = \frac{8}{\pi^2} = 0.81 = \mathbf{81\%}$$

# Diode Rectifier

## Rectifier with a Filter Capacitor

At the end of the discharge interval, which lasts for almost the entire period  $T$ ,

$$v_O = V_p - V_r,$$

where  $V_r$  is the peak-to-peak ripple voltage.

The output dc voltage ( $V_O$ ) can be obtained by taking the average values of  $v_O$ ,


$$V_O = V_p - \frac{1}{2} V_r$$

During the diode-off interval,  $v_O$  can be expressed as

$$v_O = V_p e^{-t/CR}$$

At the end of the discharge interval we have

$$V_p - V_r \cong V_p e^{-T/CR}$$

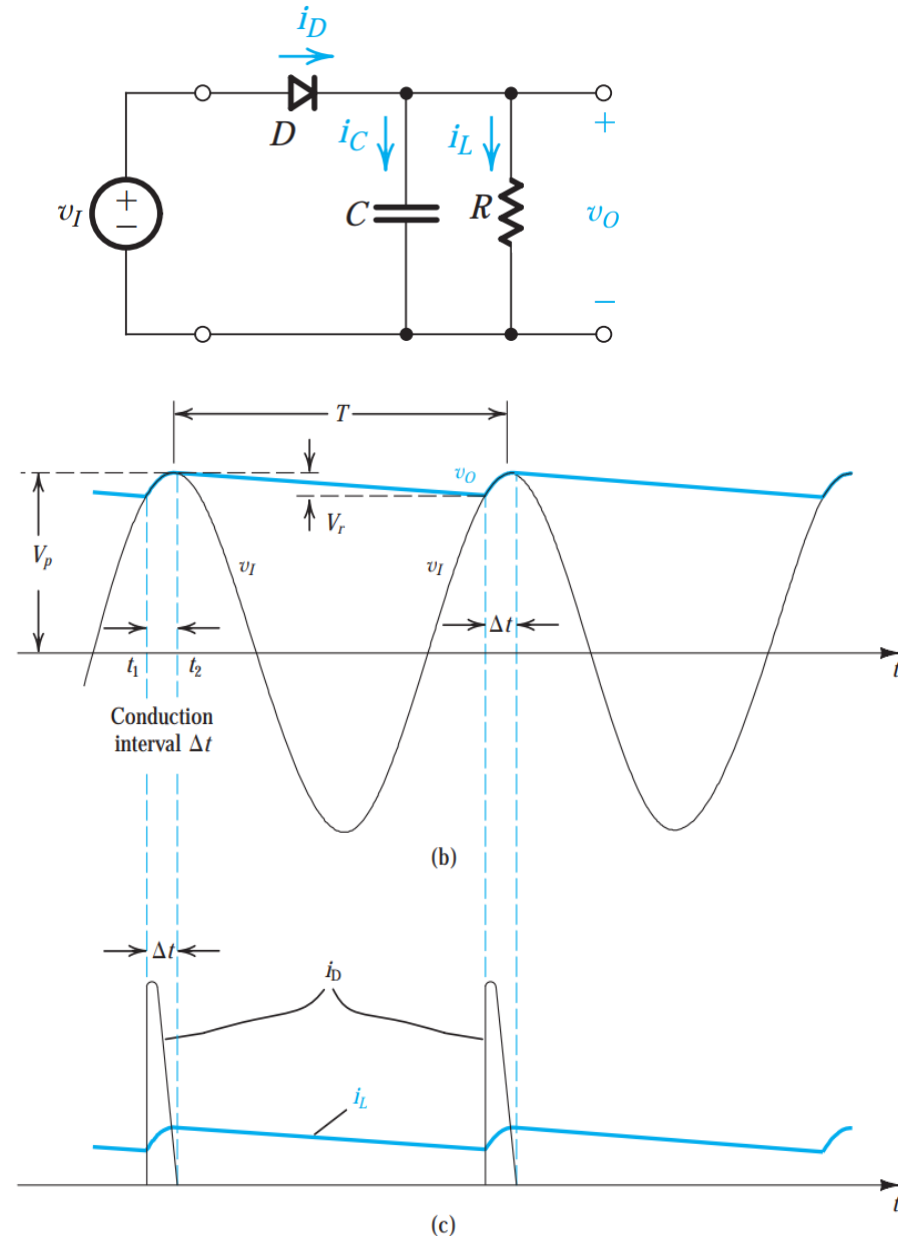

# Diode Rectifier

Now, since  $CR \gg T$ , we can use the approximation  $e^{-T/CR} \cong 1 - \frac{T}{CR}$  to obtain

$$V_p - V_r \cong V_p \left(1 - \frac{T}{CR}\right)$$

$$V_p - V_r \cong V_p - V_p \frac{T}{CR}$$

$$V_r \cong V_p \frac{T}{CR}$$

$$\therefore V_r \cong \frac{V_p}{fCR}$$

Assuming that diode conduction ceases almost at the peak of  $v_p$ , we can determine the conduction interval  $\Delta t$  from

$$V_p \cos(\omega \Delta t) = V_p - V_r$$

# Diode Rectifier

Since  $(\omega\Delta t)$  is a small angle, we can employ the approximation

$$\cos(\omega\Delta t) = 1 - \frac{1}{2}(\omega\Delta t)^2$$

$$\therefore V_p \left(1 - \frac{1}{2}(\omega\Delta t)^2\right) = V_p - V_r$$

$$\Rightarrow V_p - \frac{1}{2}V_p(\omega\Delta t)^2 = V_p - V_r$$

$$\Rightarrow \frac{1}{2}V_p(\omega\Delta t)^2 = V_r$$

$$\Rightarrow V_p(\omega\Delta t)^2 = 2V_r$$

$$\Rightarrow (\omega\Delta t) = \sqrt{\frac{2V_r}{V_P}}$$

$$\Rightarrow \Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}}$$